

PROBLEM #

NAME

1/x

GIVEN: PROBLEM STATEMENT

REQUIRED: WHAT IS REQUIRED

SOLUTION: YOUR SOLUTION

- BOX YOUR ANSWER
- DO NOT WRITE IN MARGINS
- LINES MUST BE STRAIGHT
- NO COPIES
- YOU CAN USE MATHECAD/MATLAB
- DO NOT WRITE ON BACK

GIVEN: THE CIRCUIT IN FIGURE P3.77

REQUIRED: WRITE THE NODE EQUATIONS FOR THE CIRCUIT SHOWN

SOLUTION:

$$\frac{V_1}{\bigcirc} = V_1 - V_4 - \frac{3000 I_x}{5k\Omega} + I_x + \frac{V_1 - V_2}{4k\Omega}$$

$$\frac{V_2}{\bigcirc} = \frac{V_2 - V_1}{4k\Omega} + \frac{V_2 - V_3}{2k\Omega} - 0.001 V_x$$

$$\frac{V_3}{\bigcirc} = \frac{V_3 - V_2}{2k\Omega} + \frac{V_3 - 0}{2k\Omega} + 6mA$$

$$\frac{V_4}{\bigcirc} = V_4 - V_1 + \frac{3000 I_x}{5k\Omega} + \frac{V_4 - 0}{6k\Omega} - 6mA$$

$$I_x = \frac{V_1 - 0}{6k\Omega}$$

$$V_x = V_3$$